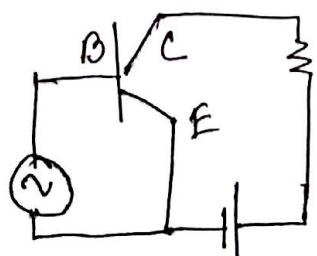


9.1 Faithful Amplification:


The process of raising the strength of a weak signal without any change in its general shape is known as "faithful Amplification".



Condition must be satisfied:

1. Proper zero signal collector current
 2. Minimum proper base-emitter voltage
 3. Minimum proper collector-emitter voltage. (V_{CE})
1. Proper zero signal collector current:



age ↑


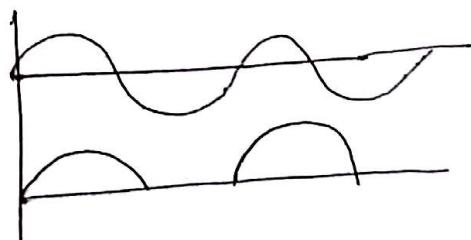


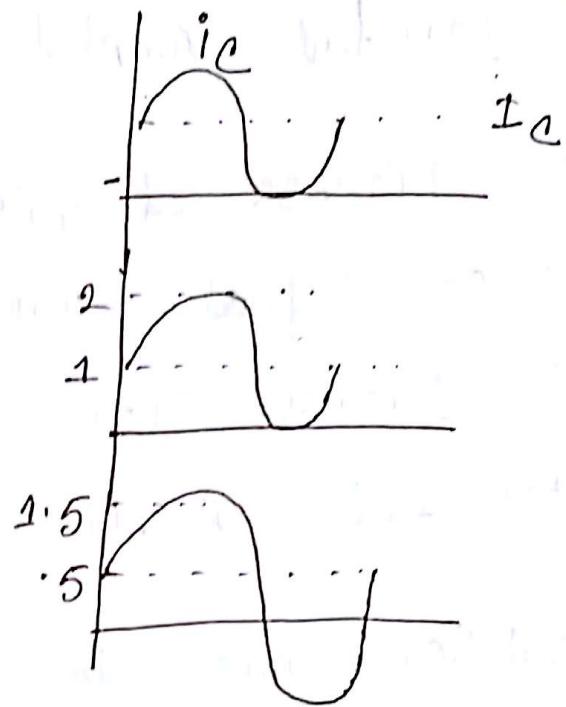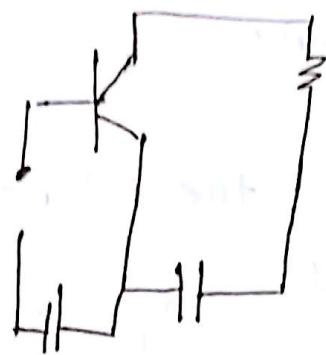



$$i = I_C + i_Q \rightarrow AC$$

$\rightarrow DC$

ii) Proper minimum V_{BE} :

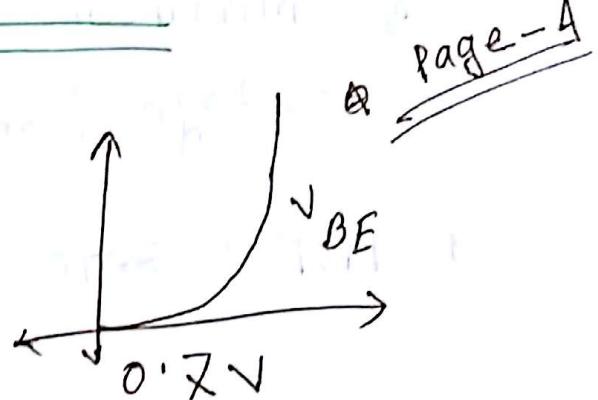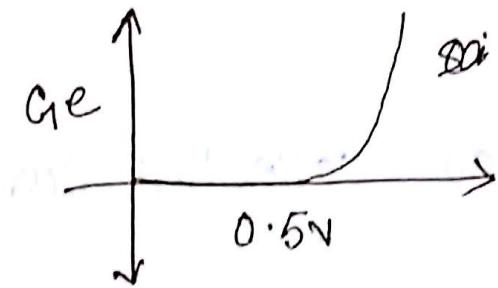

iii) Proper minimum V_{CE} :

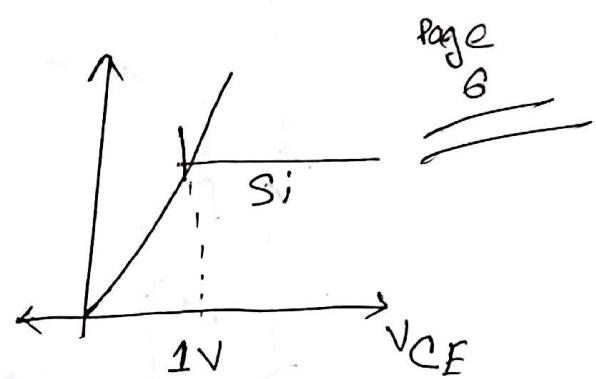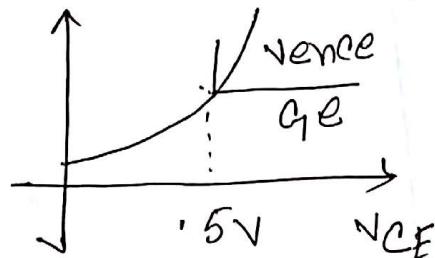

page
6

page
7

9.2:

Biasing def.: Biasing

9.7 Method of Biasing:


i) Base Resistor

page - 8

ii) Voltage divider bias.

9.8 Base Resistor method:

page - 9

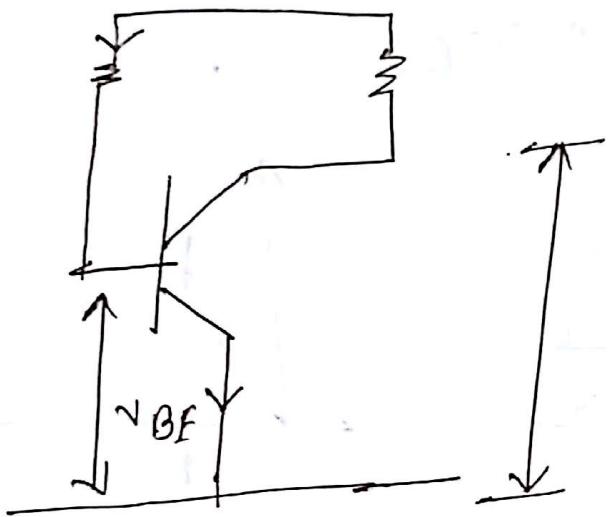

Circuit Analysis:

$$I_B = \frac{I_C}{\beta}$$

Page : 10

Applying KVL:


$$-V_{CC} + I_B R_B + V_{BE} = 0$$

$$\Rightarrow I_B R_B = V_{CC} - V_{BE}$$

$$\Rightarrow R_B = \frac{V_{CC} - V_{BE}}{I_B}$$

9.12:

ii) voltage divider method bias.

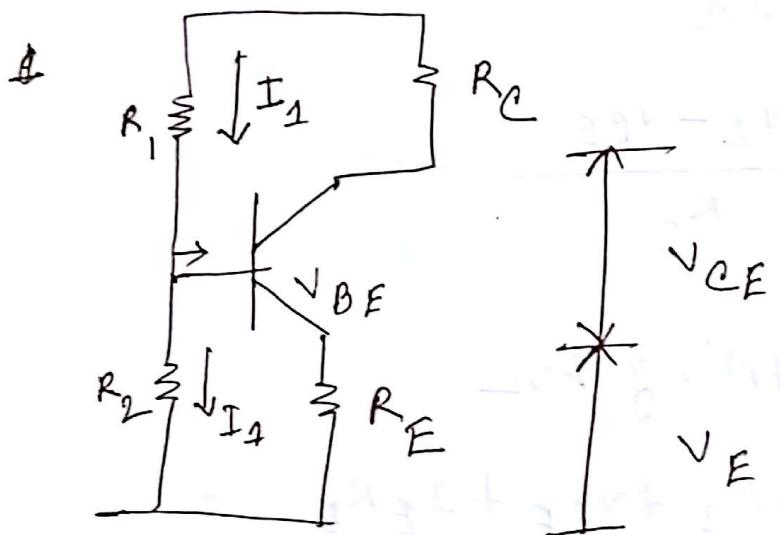

Page: 11

$$I_1 = \frac{V_{CC}}{R_1 + R_2}$$

$$V_2 = \left(\frac{V_{CC}}{R_1 + R_2} \right) \times R_2$$

Now Applying KVL,

$$-V_2 + V_{BE} + V_E = 0$$

$$\Rightarrow V_2 = V_{BE} + V_E \quad [V_E = I_E R_E]$$

$$\Rightarrow I_E = \frac{V_2 - V_{BE}}{R_E}$$

$\therefore I_E \approx I_C$

$$I_C = \frac{V_2 - V_{BE}}{R_E}$$

V_{CE} : Applying KVL

$$-V_{CE} + I_C R_C + V_{CE} + I_E R_E = 0$$

$$\begin{aligned}\Rightarrow V_{CC} &= I_C R_C + V_{CE} + I_E R_E \\ &= V_{CE} + I_C (R_C + R_E)\end{aligned}$$


$$\Rightarrow V_{CC} = V_{CE} + I_C (R_C + R_E)$$

$$\therefore V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Chapter 10

single stage transistor amp:

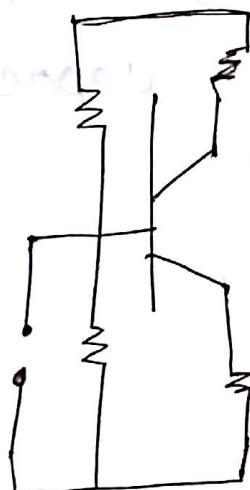when only one transistor is used with associated circuiting to amplify a weak signal, it is called "single Transistor Amplifier"




Page - 16

10.4:

Practical circuit:

Page - 16

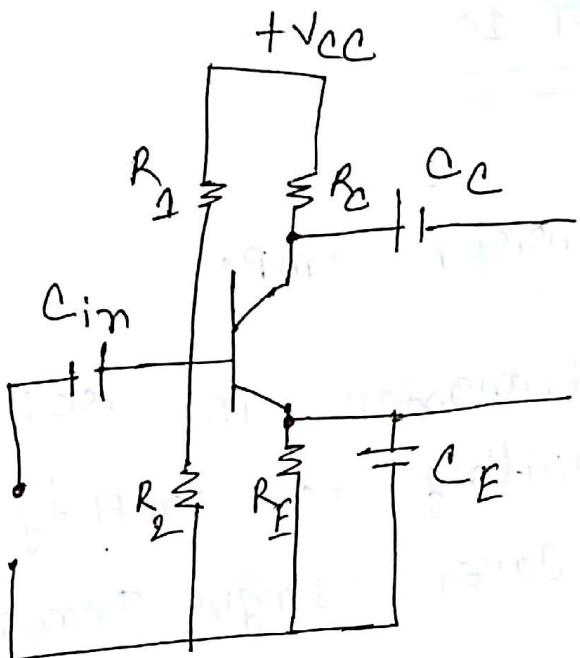

i) Biasing circuit,
(R_1, R_2, R_E)

ii) Input capacitor, C_{in}

iii) Emitter bypass capacitor, C_E

iv) Coupling capacitor, C_C

Emitter current:

$$i_E = \text{I}_E + i_e$$

Base current:

$$i_B = I_B + i_c$$


Collector current:

$$i_C = I_C + i_c$$

Chapter - 11

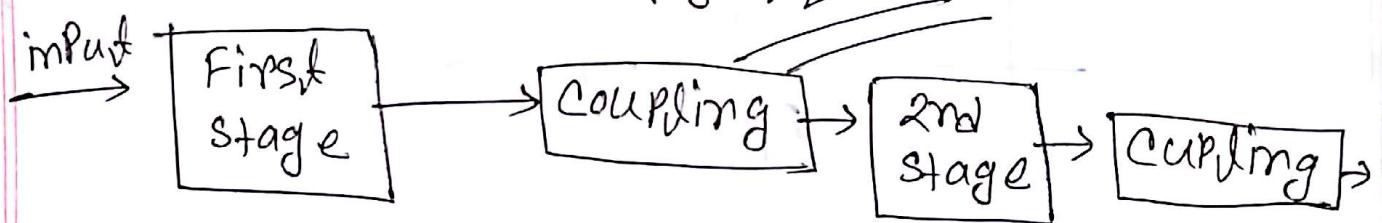11.1

A Transistor containing more than one stage of amplification is known as "multistage transistor Amplifier".
Page : 22




11.3

Gain: The ratio of output quantity to the input one is called Gain.

$$G = G_1 \times G_2 \times G_3 \times \dots$$

$$G_1 = \frac{O/P}{I/P}$$

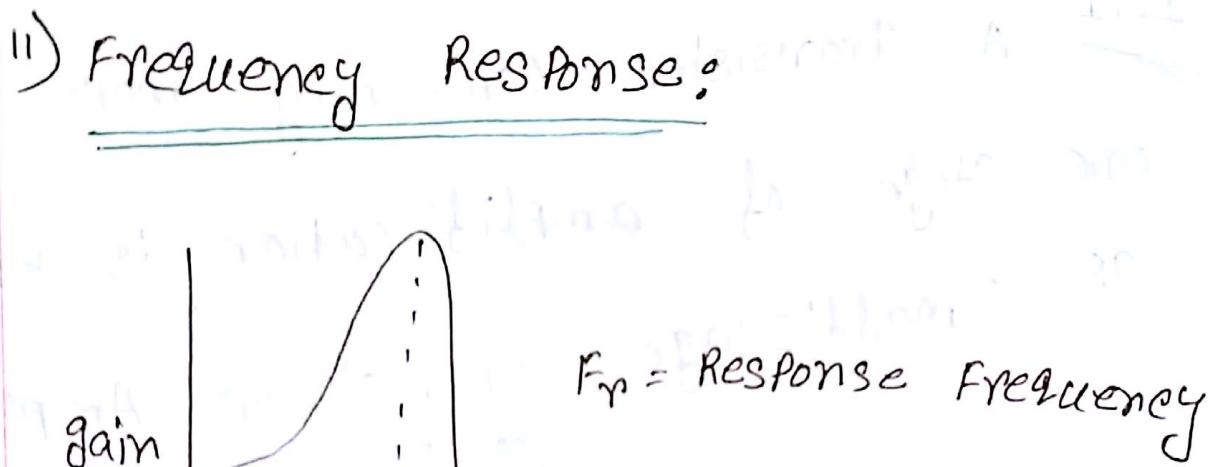

III) Decibel gain:

The common logarithm (base 10 of Power)

Gain known as bel power gain

$$\text{Power gain} = \log_{10} \frac{P_{\text{out}}}{P_{\text{in}}} \text{ bel}$$

$$1 \text{ bel} = 10 \text{ dB}$$


$$\therefore \text{Power gain} = 20 \log_{10} \frac{P_{\text{out}}}{P_{\text{in}}} \text{ dB}$$

$$\therefore \text{Voltage gain} = 20 \log_{10} \frac{V_{\text{out}}}{V_{\text{in}}} \text{ dB}$$

$$\therefore \text{Current gain} = 20 \log_{10} \frac{I_{\text{out}}}{I_{\text{in}}} \text{ dB}$$

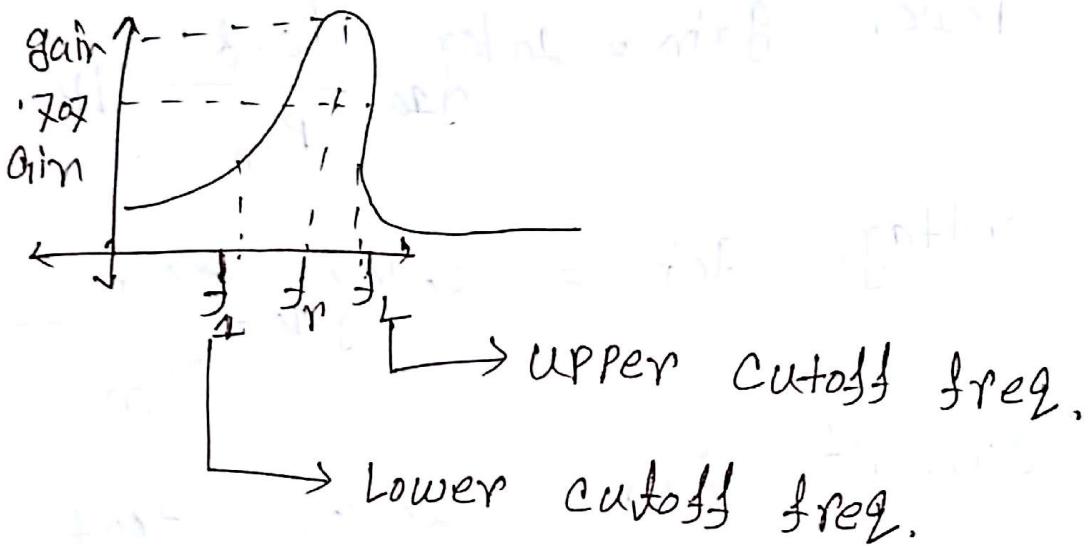iv) Bandwidth:

The range of frequency over which the voltage gain is equal to or greater than 70.7% of max gain is known as "Bandwidth".



Full in voltage from max gain =


$$20 \log_{10} 100 - 20 \log_{10} 20.7$$

$$= 20 \log_{10} \frac{100}{20.7}$$

$$= 20 \log_{10} 1.4142 = 3 \text{ dB}$$

11.5

RC Coupled transistor Amplifier.

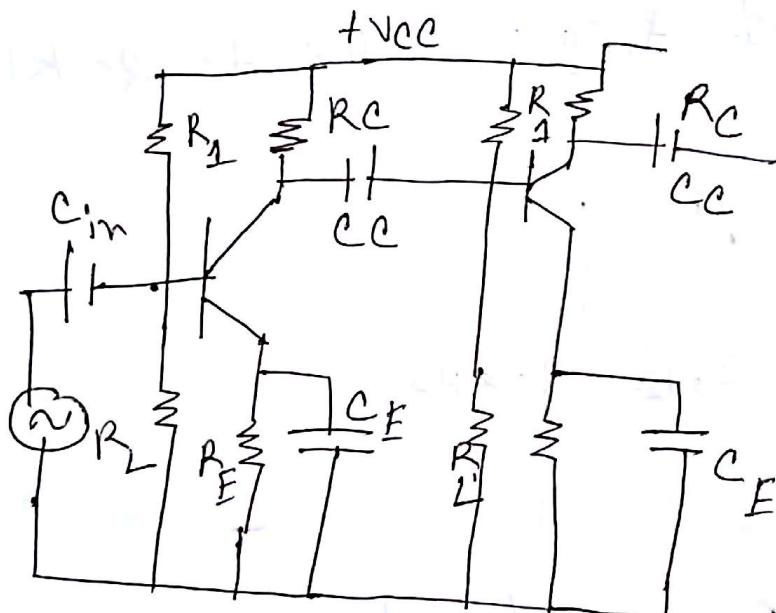

Page 29


Frequency Response:

- I) At low freq : -250 Hz gain
→ C_C is very high
→ C_E cannot shunt
- II) At high freq : > 20 kHz

→ C_C is very small.

→ Capacitive reactance is very low.

''' At mid freq: (50 Hz to 20 kHz)

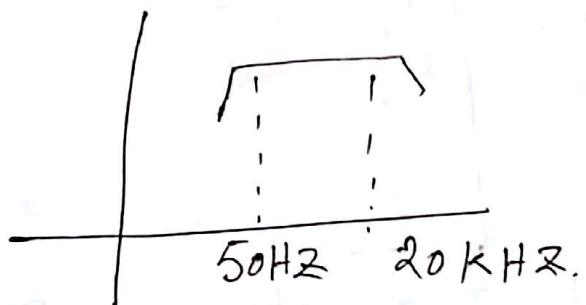

Adv: i) Excellent frequency

ii) Lower cost

iii) circuit is compact


Dis Adv:

i) Low voltage gain


ii) noisy with age

iii) Impedence matching is poor

Chapter: 13

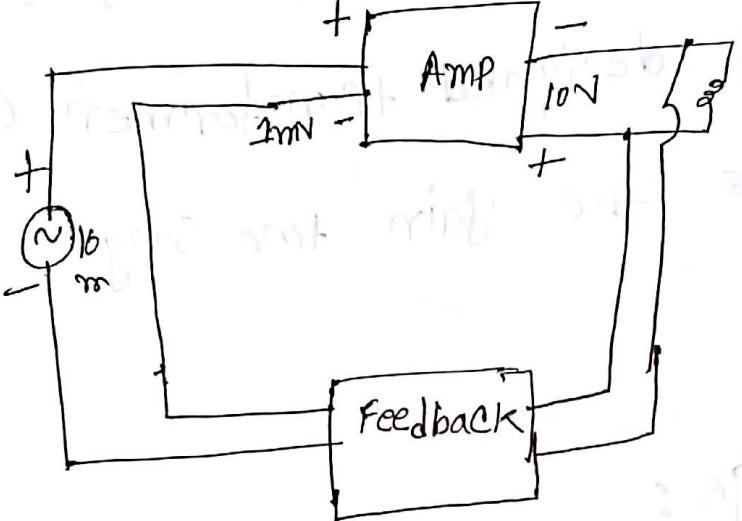

13.3^o gain of negative feedback:

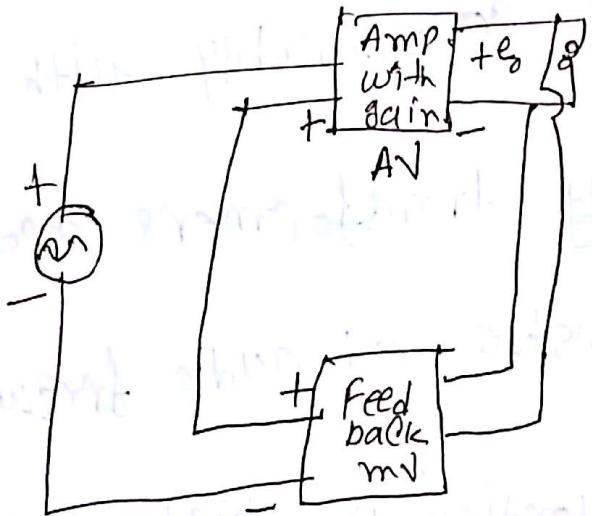

Page 52

Actual input to amp = $e_g - m_V e_o$

$$\therefore (e_g - m_V e_o) A_V = e_o$$

$$\Rightarrow A_V e_g - A_V m_V e_o = e_o$$

$$\Rightarrow e_o (1 + A_V m_V) = A_V e_g$$

$$\Rightarrow \frac{e_o}{e_g} = \frac{A_V}{1 + A_V m_V}$$

$$\Rightarrow A_{Vf} = \frac{A_V}{1 + A_V m_V}$$

Math

$$A_V = 3000$$

$$m_V = 0.01$$

$$A_{Vf} = ?$$

$$V = 20 \log \frac{V_{out}}{V_{in}}$$

$$I = 20 \log \frac{I_{out}}{I_{in}}$$

Left - New
Right - Old

$$13.2 - 13.8$$

Math

Ch-14



14.1 : oscillator: An electronic device that generates sinusoidal oscillations of desired frequency is known as oscillator.

Adv:

- 1) Non rotating device
- 2) Quite silent.
- 3) Frequency range is good (20 Hz to 1 MHz)
- 4) Good frequency stability.



14.2 damped oscillation:

undamped oscillation:

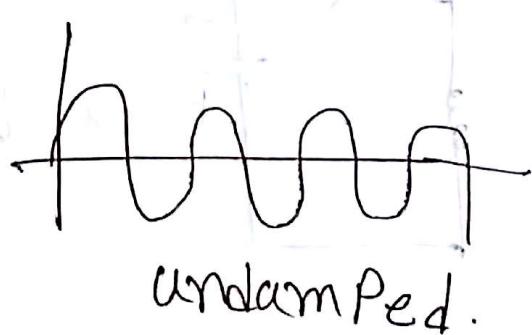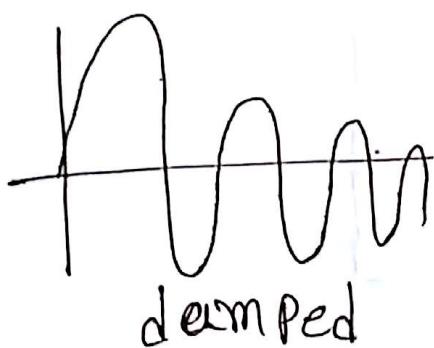


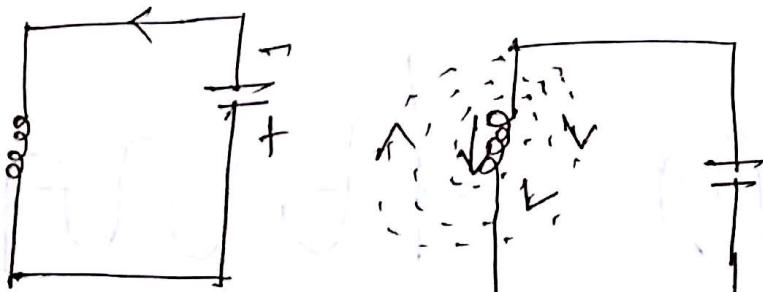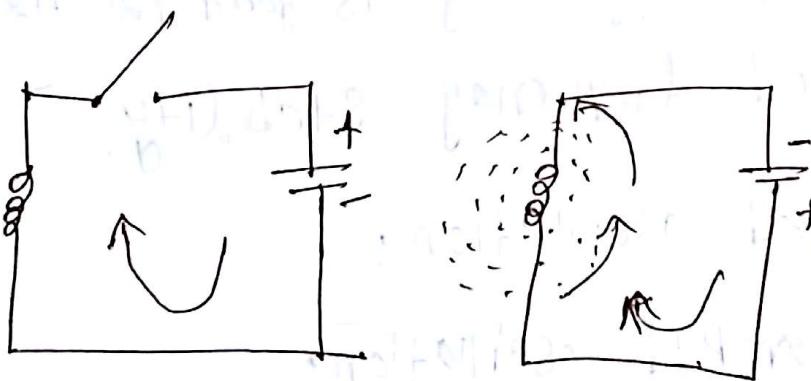14.3^o oscillatory circuits


A circuit that produces electrical oscillations of desired frequency is known as oscillatory circuit or tank circuit.



14.10

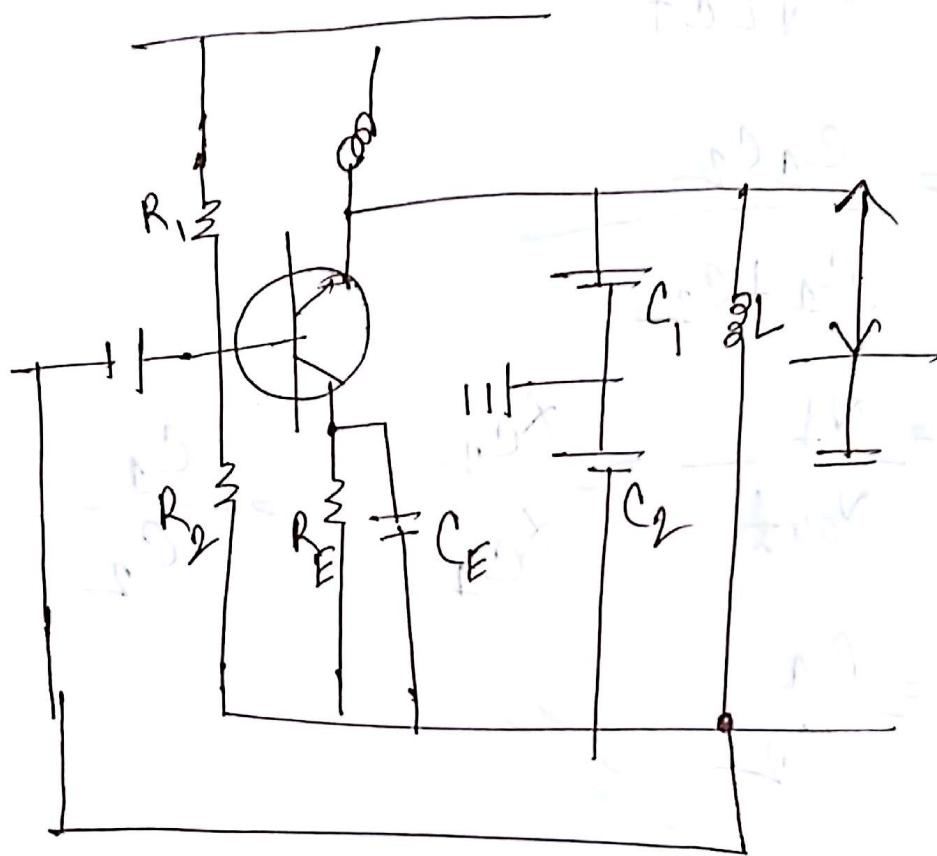

output:

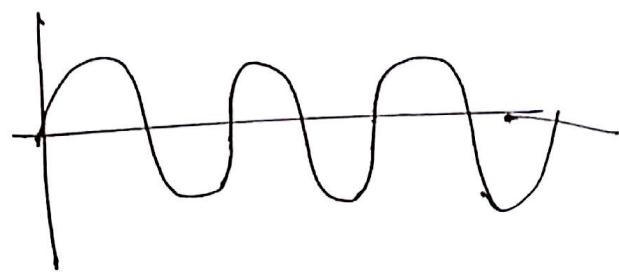

$$f = \frac{1}{2\pi \sqrt{LC}}$$

$$C_2 = \frac{C_1 C_2}{C_1 + C_2}$$

$$MV = \frac{V_f}{V_{out}} = \frac{X_{C_2}}{X_{C_1}} = \frac{C_1}{C_2}$$

$$MV = \frac{C_1}{C_2}$$