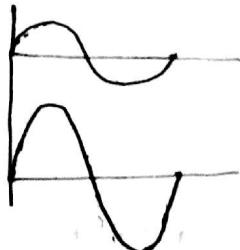




Electrical Devices and Circuits



Final exam:chapter-9, 10, 11, 13, 14, Opampfrom midterm: chapter-8 (lecture-3),
chapter-6 (lecture-2),Chapter: 99.1Faithful amplification:

The process of rising the strength of a weak signal without changing its general shape is known as faithful amplification.



Condition must be fulfilled:

- (i) proper zero signal collector current.
- (ii) minimum proper base-emitter voltage.
- (iii) minimum proper collector-emitter voltage.

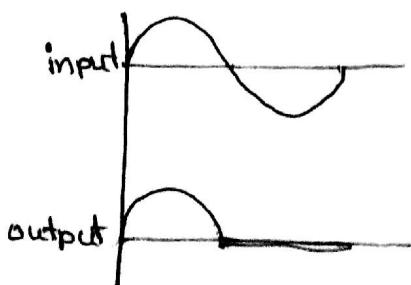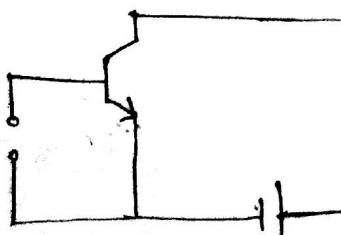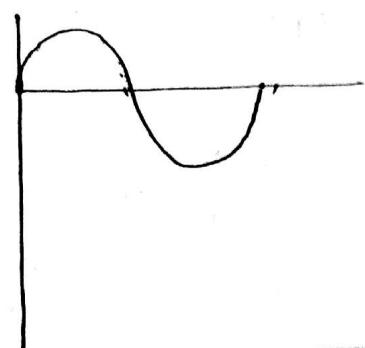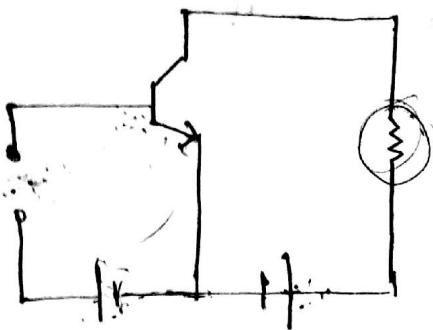
(i) proper zero signal collector current:



$$i_C = i_{c'} + I_c$$

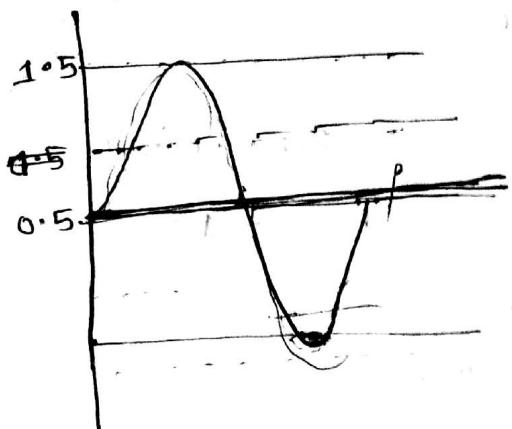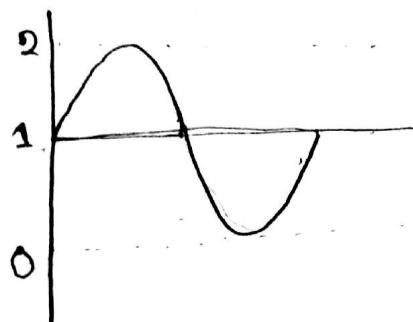


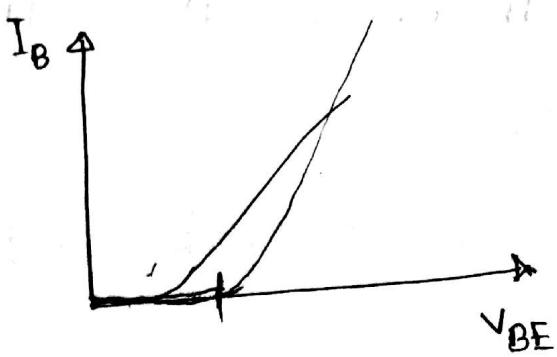(ii) minimum proper base-emitter voltage:



0.7V - Si
0.3V - Ge

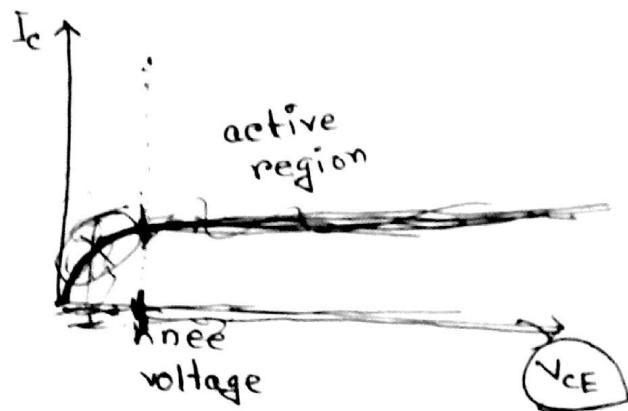(iii) proper minimum collector-emitter current:



$$G_{re} = 0.5 \text{ V}$$


$$S_i = 1 \text{ V}$$

9.2

The proper flow of zero signal [collector current] and maintaining proper [collector-emitter voltage] is called Transistor biasing.

9.8

Base resistor method:

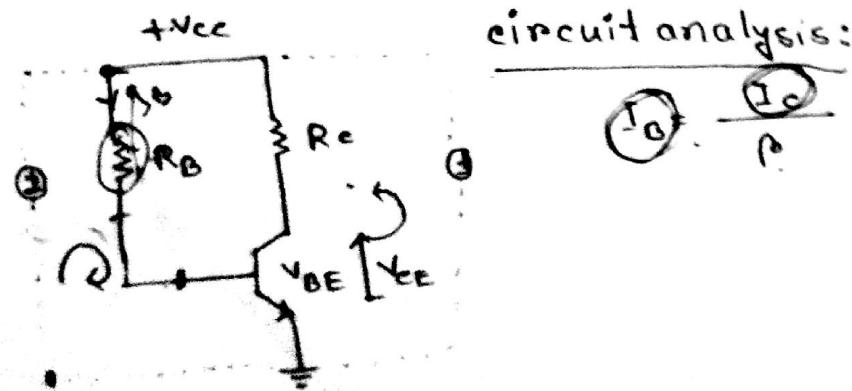

Now using KVL,

$$-V_{CC} + I_B R_B + V_{BE} = 0$$


$$\text{or, } I_B R_B + V_{BE} = V_{CC}$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$\text{or, } R_B = \frac{V_{CC} - V_{BE}}{I_B}$$

Q. 12

Voltage divider bias method:

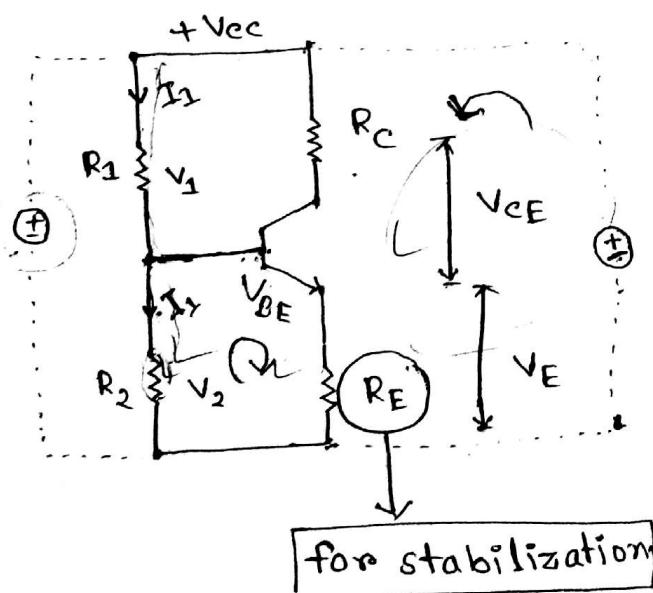

Circuit analysis: (Ic)

$$(i) I_1 = \frac{V_{CC}}{R_1 + R_2}$$

voltage across R_2 ,

$$V_2 = \frac{V_{CC}}{R_1 + R_2} \times R_2$$

Now, using KVL —

$$V_2 = V_{BE} + V_E$$

$$\text{or, } V_2 = V_{BE} + I_E R_E$$

$$I_E = \frac{V_2 - V_{BE}}{R_E}$$

$$\therefore I_E \approx I_c$$

$$\therefore I_C = \frac{V_2 - V_{BE}}{R_E}$$

(ii) V_{CE}

using KVL,

$$-V_{CC} + I_e R_e + V_{CE} + V_E = 0$$



$$\text{or, } -V_{CC} + I_e R_e + V_{CE} + I_E R_E = 0$$

$$\text{or, } -V_{CC} + I_e R_e + V_{CE} + I_e R_E = 0 \quad [\because I_e = I_E]$$

$$\text{or, } \boxed{V_{CE} = V_{CC} - I_e (R_e + R_E)}$$

Chapter-10Signal stage Transistor Amplifier:10.1

when only one transistor is used for amplifying a weak signal, the circuit is known as signal stage transistor amplifier.

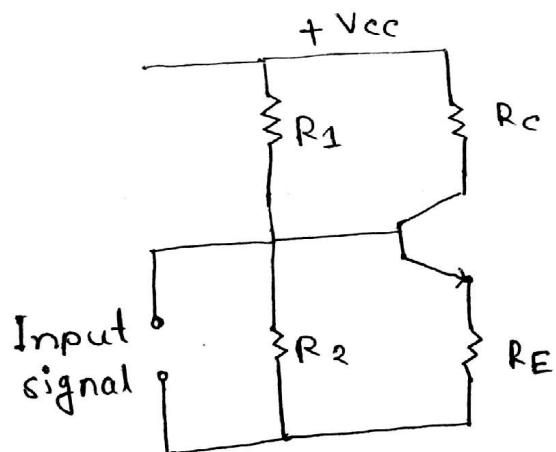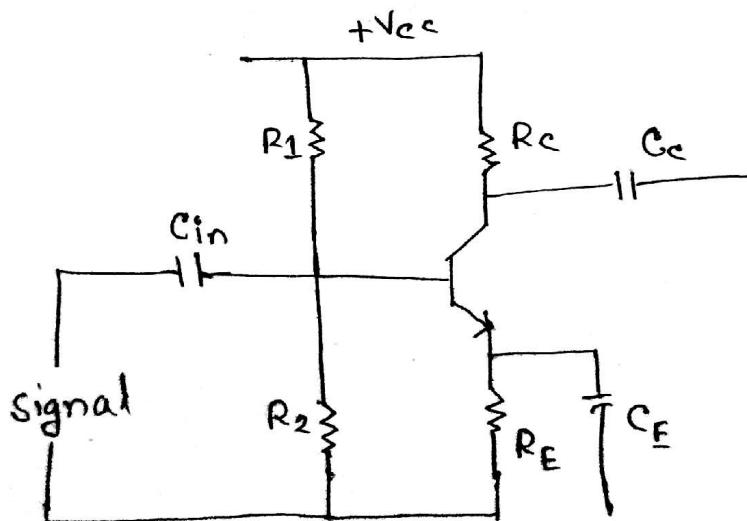10.4practical circuit of single stage:

- (i) Biasing circuit
- (ii) Emitter bypass capacitor
- (iii) Input capacitor
- (iv) Coupling capacitor

$$* \text{Base current: } i_B = I_B + i_b$$

$$* \text{Collector current: } i_C = I_C + i_c$$

$$* \text{Emitter current: } i_E = I_E + i_e$$


24.07.2017

CSE-224


Electrical Devices and Circuits

Chapter-11

A transistor circuit containing more than one stage of amplification is known as "Multistage transistor amplifier."

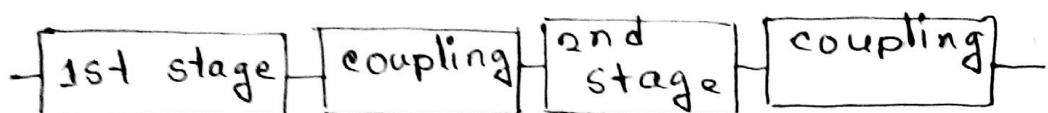11.2

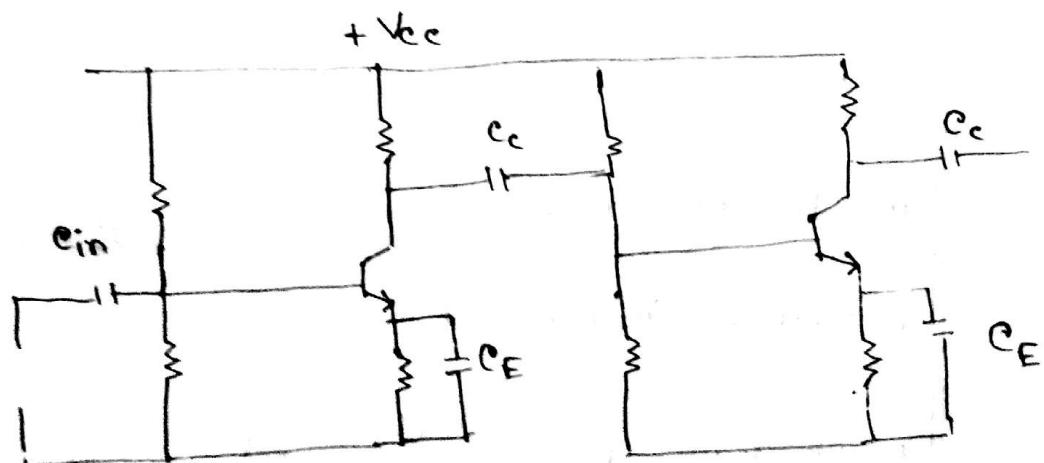- (i) bypass capacitor
- (ii) coupling capacitor




(2)

11.3

(i) Gain: The ratio of the output to the input of the amplifier is called Gain of amplifier.

$$G = G_1 \times G_2 \times G_3 \times \dots$$

(ii) Frequency Response:

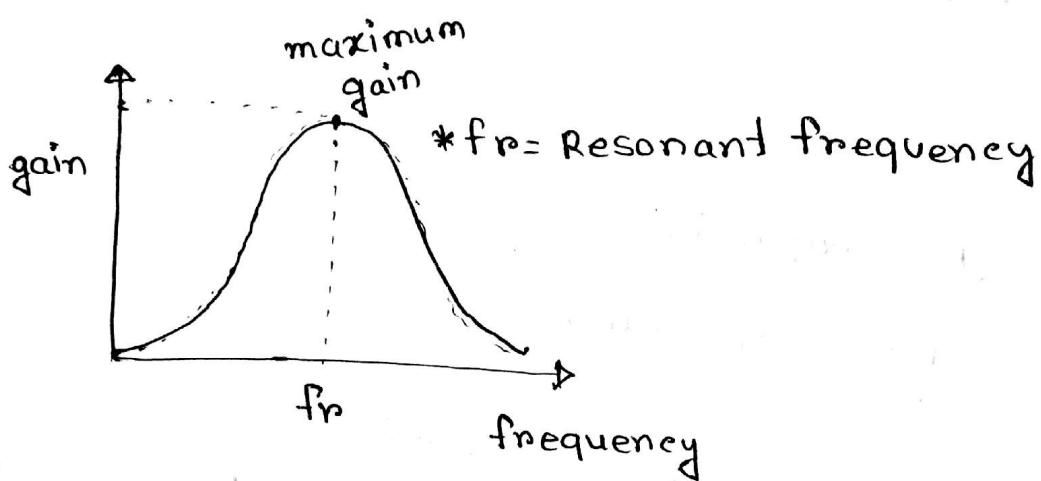

(iii) Decibel Gain: The common logarithm of power gain is called bel power gain.

$$\text{power gain} = \log \frac{P_{\text{out}}}{P_{\text{in}}} \text{ bel}$$


$$1 \text{ bel} = 10 \text{ dB}$$

$$\therefore \text{Power gain} = 10 \log_{10} \frac{P_{\text{out}}}{P_{\text{in}}} (\text{dB})$$

$$\boxed{\text{Voltage gain} = 20 \log_{10} \frac{V_{out}}{V_{in}}} \quad * * *$$

$$\boxed{\text{Current gain} = 20 \log_{10} \frac{I_{out}}{I_{in}}}$$

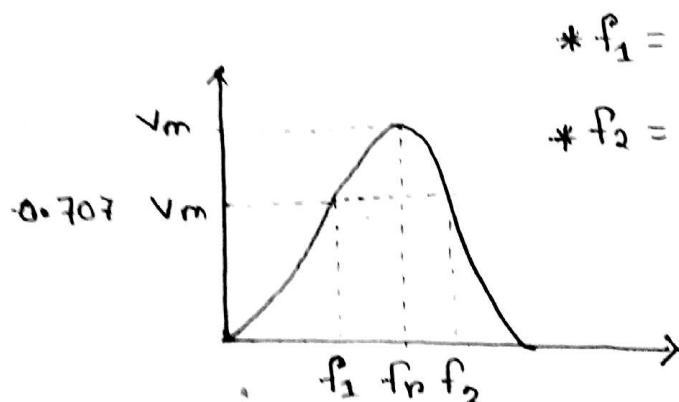(iv) Bandwidth: The range of frequency over which the voltage gain is equal to or greater than 70.7% of the maximum gain is called Bandwidth.



* f_1 = Lower cut off frequency


* f_2 = Higher cut off frequency

$$\begin{aligned}
 \text{Fall in voltage gain} &= 20 \log_{10} 100 - 20 \log_{10} 70.7 \\
 &= 20 \log_{10} \frac{100}{70.7} \\
 &= 20 \log_{10} 1.4142 \\
 &= 3 \text{ dB}
 \end{aligned}$$

3 dB frequency / Half power frequency

11.5

* RC means resistance capacitor

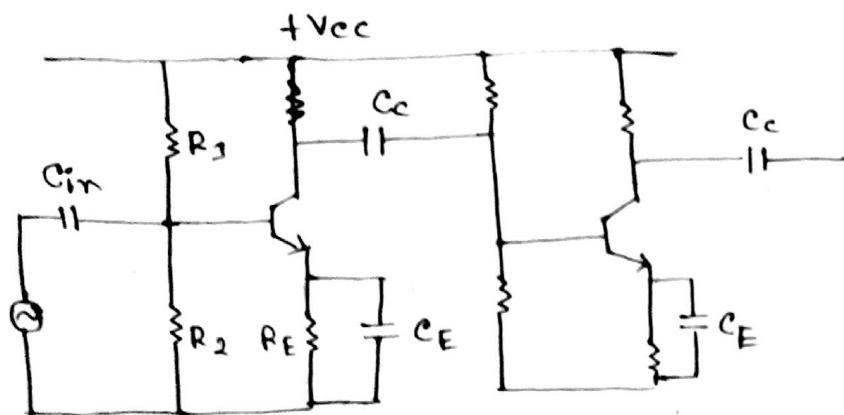RC coupled transistor amplifier:Operation:

- (i) effective load resistance.
- (ii) loading effect.

Frequency response:

(i) At lower frequency < 50 Hz

$$\rightarrow C_C \text{ quite high } [X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}]$$


$\rightarrow C_E$ cannot shunt

(ii) At Higher frequency > 20 kHz

$\rightarrow C_C$ is very small

$\rightarrow C_E$ Base current \uparrow , $\beta \downarrow$

(iii) Mid frequency (50 Hz to 20 kHz)

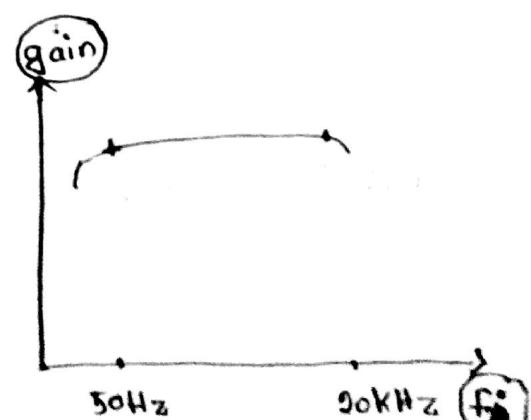


8
Electronic Devices and CircuitsRC coupled:Advantages:


- (i) It has excellent frequency response.
- (ii) It has lower cost.
- (iii) Circuit is very compact.

Disadvantages:

- (i) Low voltage and power gain.
- (ii) Noisy with age.
- (iii) Impedance matching is poor.

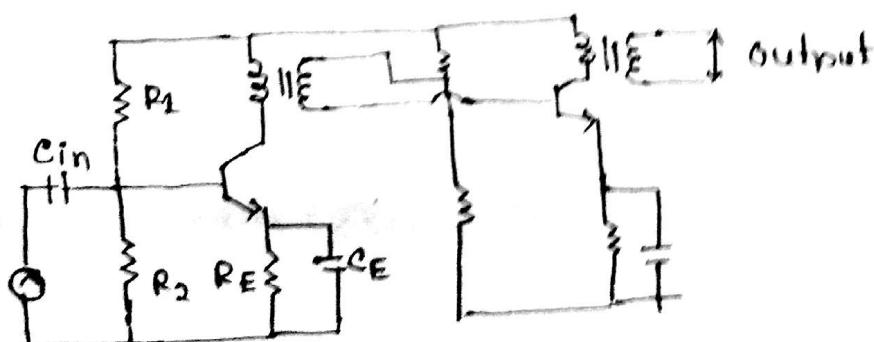12.6Transformer coupled transistor amplifier:Operation:

Frequency response:

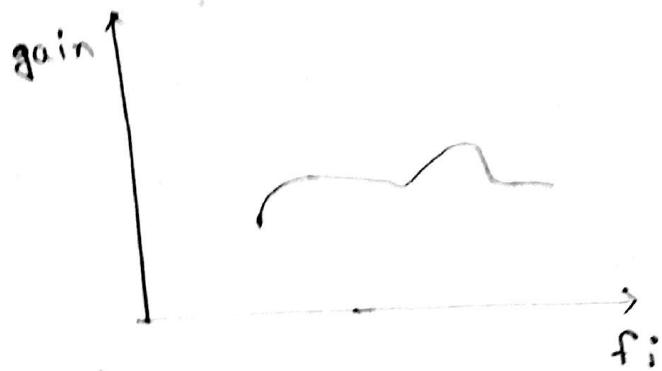

advantage:

- (i) no signal power is lost
- (ii) Excellent impedance matching
- (iii) Higher gain

disadvantage:

- (i) poor frequency response
- (ii) Bulky and expensive
- (iii) Frequency distortion is higher.

math

$$\underline{13 \cdot 1 - 13 \cdot 8}$$

$$14 \cdot 3 - 14 \cdot 6$$

Chapter-13


13.1
13.2
13.3

Negative feedback:13.1


The process of injecting a function of output of energy by some device is called feedback.

(i) positive feedback:


180° phase shift

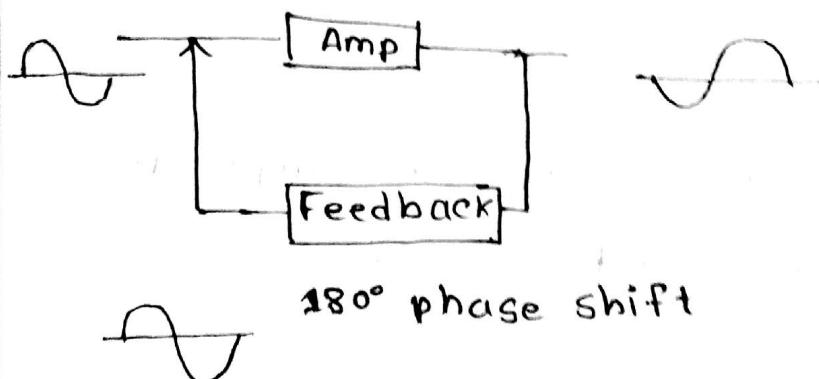common emitter(ii) Negative feedback:

180° phase shift

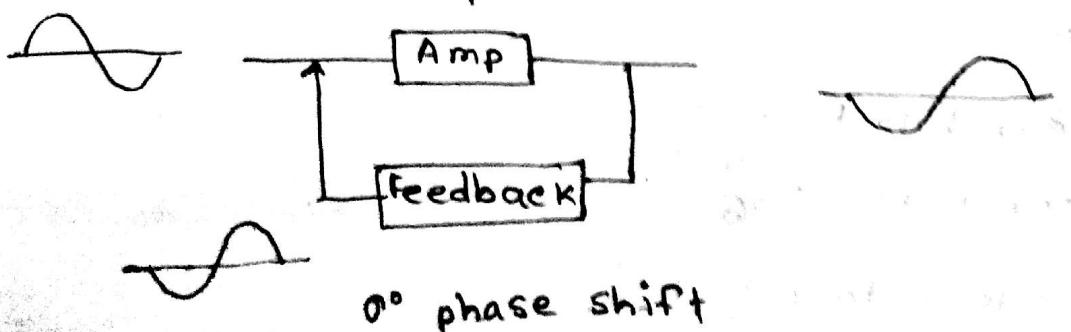

13.2

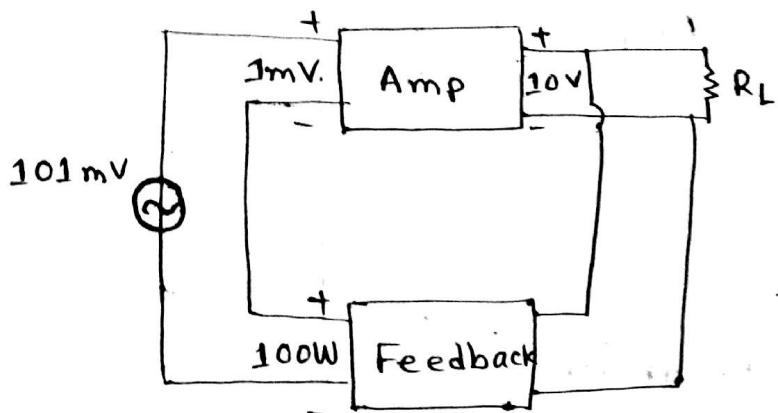

Gain of amplifier without feedback,

$$A_v = \frac{10V}{1mV} = 10,000$$

Gain of amplifier with feedback, $A_{vf} = \frac{10V}{101mV}$


$$= 100$$

Fraction of output, $m_v = \frac{100 mV}{10 V}$

$$= 0.01$$

13.3

Gain of negative feedback:

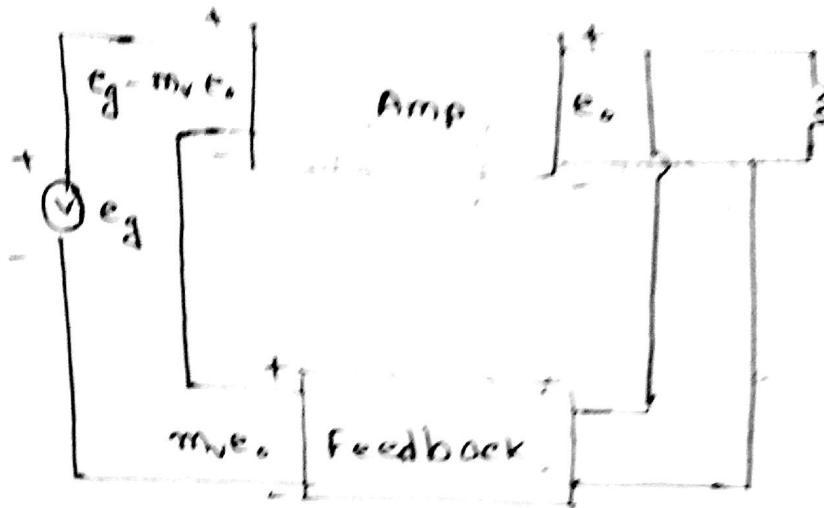

Now,

Actual input to amplifier = $e_g - m_v e_o$

$$\text{or, } (e_g - m_v e_o) A_v = e_o \quad \text{now, } A_v = \frac{e_o}{e_g - m_v e_o}$$

$$\text{or, } A_v e_g - A_v m_v e_o = e_o$$

$$\text{or, } e_o (1 + A_v m_v) = A_v e_g$$

$$\text{or, } \frac{e_o}{e_g} = \frac{A_v}{1 + A_v m_v}$$

$$\therefore A_{vf} = \frac{A_v}{1 + A_v m_v} \quad ***$$

Chapter- 14

Oscillator

14.1
14.2
14.3
14.10
14.11


14.1

Oscillator:


An electronic devices that generates sinusoidal oscillation of desired frequency is called "oscillator".

Advantages:

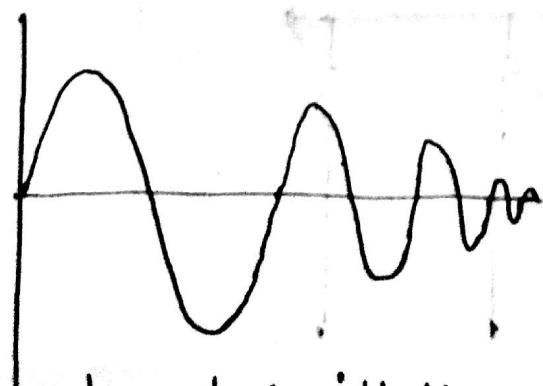- i) Non rotating device *Alternator
- ii) Quite silent
- iii) Range higher (from small to higher)
- iv) High efficiency




damped oscillation

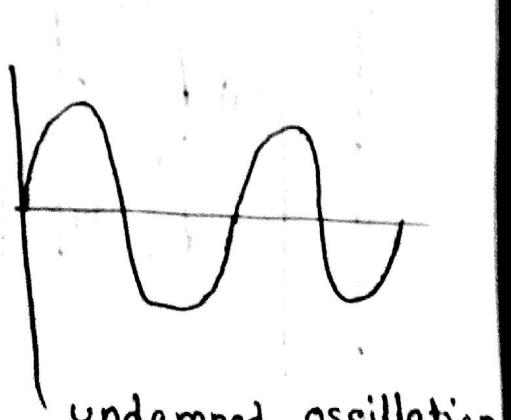

undamped oscillation

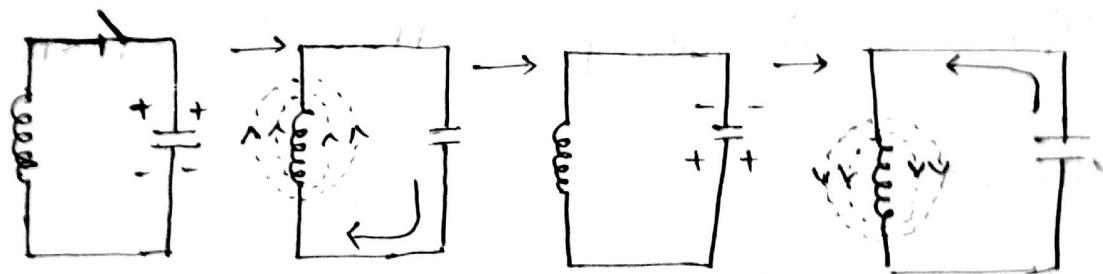
14.3

Oscillatory circuit: A circuit which produces electrical oscillations of any desired frequency is known as oscillatory circuit or tank circuit.



14.10

Colpitts Oscillator:

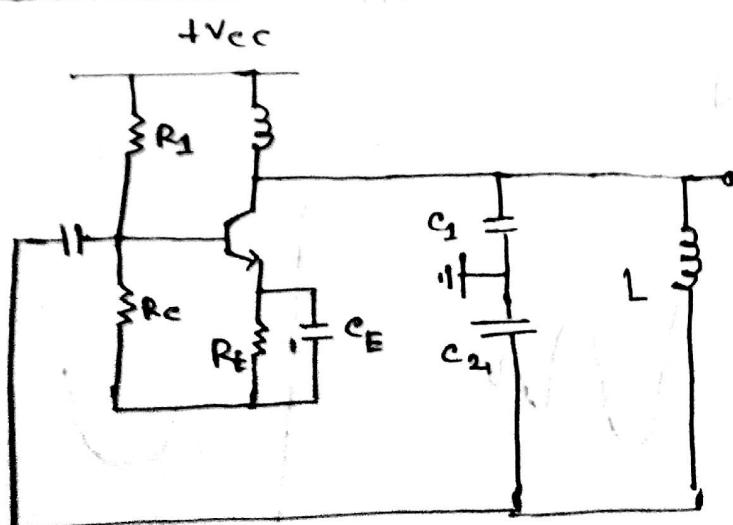

Operation:

$$f = \frac{1}{2\pi \sqrt{LC_T}}$$

$$C_T = \frac{C_1 C_2}{C_1 + C_2}$$


Feedback fraction:

$$m_v = \frac{V_f}{V_{out}} = \frac{x_{c_2}}{x_{c_1}} = \frac{C_1}{C_2}$$

$$\therefore m_v = \frac{C_1}{C_2}$$

14.11

Hartley oscillator:

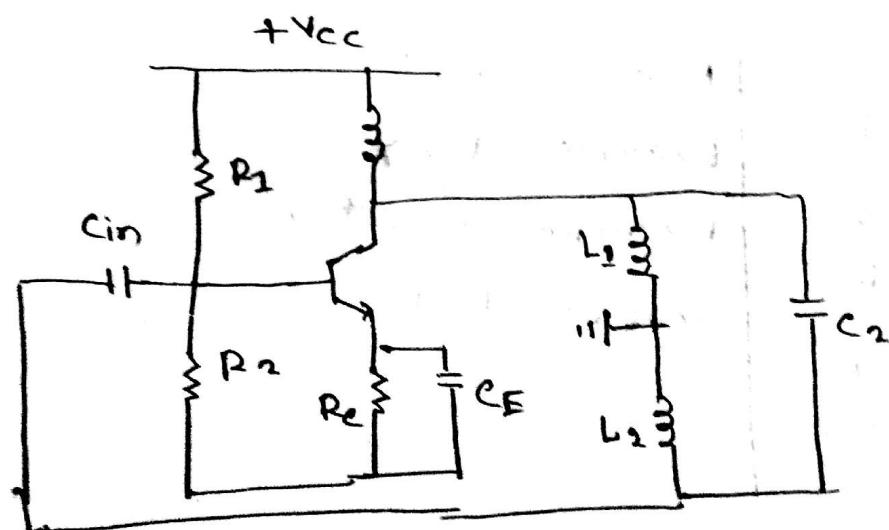

operation:

$$f = \frac{1}{2\pi \sqrt{L_T C}}$$

$$L_T = L_1 + L_2 + 2M$$

Feedback fraction:

$$\begin{aligned} m_v &= \frac{V_f}{V_{out}} \\ &= \frac{X_{L_2}}{X_{L_1}} \\ &= \frac{L_2}{L_1} \end{aligned}$$

$$m_v = \frac{L_2}{L_1}$$

Example - 14.3

Example - 14.4

Example - 14.5

Example - 14.6

Example - 13.1

Example - 13.2

Example - 13.3

Example - 13.4

Assignment

1. what is faithful amplification?
describe all the criteria it needs to fulfill.
2. Describe voltage divider bias method
3. Describe Single stage transistor amplifier
4. Describe transformer coupled amplifier
5. Describe Hartley oscillator

Example - 13.5

Example - 13.7

Example - 13.8*

Example - 13.6